

H

Roll No. 2399001

TCS-308

B. TECH. (CSE) (THIRD SEMESTER) MID SEMESTER

EXAMINATION, Dec., 2023

LOGIC DESIGN AND COMPUTER
ORGANIZATION

Time : 1½ Hours

Maximum Marks : 50

Note : (i) Answer all the questions by choosing any *one* of the sub-questions.

(ii) Each sub-question carries 10 marks.

1. (a) Minimize the following using Karnaugh map : (CO1)

$$F = \sum m(1, 4, 7, 10, 13) + \sum d(5, 14, 15)$$

$$F = \pi M(0, 2, 4, 7, 8, 10, 12)$$

OR

- (b) Reduce the expression : (CO1)

$$(i) F = \overline{AB} + \overline{A} + AB$$

$$(ii) F = (B+BC)(\overline{B}+BC)(B+C)$$

P. T. O.

2. (a) Reduce the following function using tabular method : (CO1)

$$F = \sum m(0, 1, 2, 8, 10, 11, 14, 15)$$

OR

- (b) Why multiplexer is called data selector ?

Realize the logic function $F(A, B, C, D)$

$$= \sum m(2, 4, 6, 7, 9, 10, 11, 12, 15) \text{ using :}$$

(CO1)

(i) 16:1 MUX

(ii) 8:1 MUX

3. (a) Explain SR F-F and discuss problems of Master Slave Flip-Flop. (CO1)

OR

- (b) Differentiate encoder and decoder. Design a BCD to Gray code converter. (CO1)

4. (a) What is the general procedure of designing a combinational circuit ? Using the procedure steps design a adder. (CO2)

(3)

OR

(b) Convert the following : (CO2)

(i) SR to T

(ii) D to JK

5. (a) Design a mod-6 synchronous counter using JK flip-flop. (CO2)

OR

(b) Differentiate between the following : (CO2)

(i) Combinational and Sequential circuits

(ii) Synchronous and Asynchronous circuits