

# B.Tech Mid Semester Examination 2023

Name of the course: B.Tech  
Name of the Paper: Basic Electrical Engineering



Semester: 1  
Course Code: TEE-107



Time: 1:30 Hrs

Maximum Marks: 50

Note:

- Answer all the questions by choosing any one of the sub questions.
- Each question carries 10 marks.

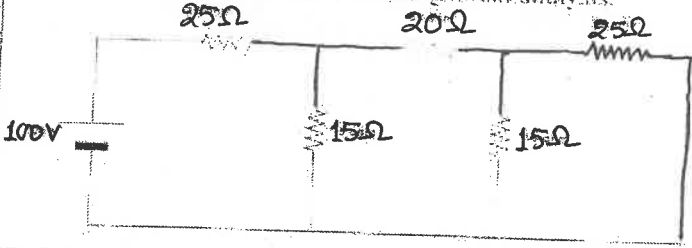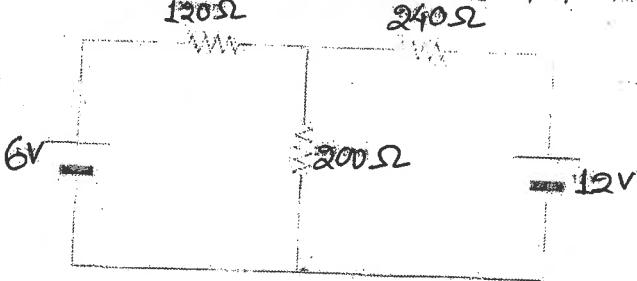Q1	(10 marks)	CO 1
a)	Write short note on: (a) Kirchhoff's Law with examples (b) Ohm's Law	
	OR	CO 1
b)	Calculate Current in all resistors using nodal analysis. 	
Q2	(10 marks)	CO 2
a)	Define: a) Charge b) Electric current c) Power d) Network & e) Circuit.	
	OR	CO 2
b)	Calculate current in 240 ohm resistor using Superposition theorem. 	
Q3	(10 marks)	CO 2

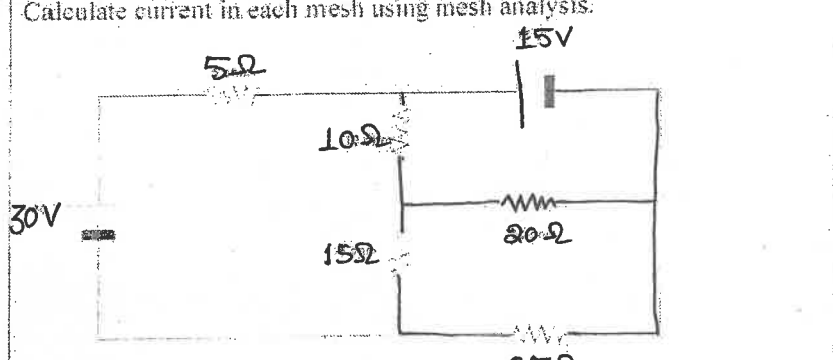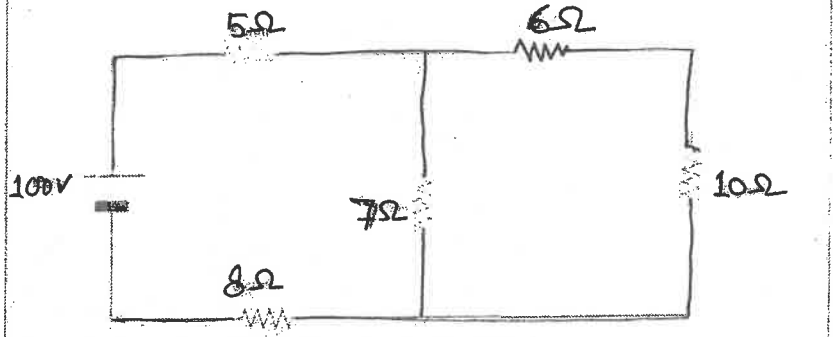a)	<p>Calculate current in each mesh using mesh analysis.</p> 	
OR		
b)	<p>State the Superposition theorem and write steps to solve the superposition theorem using suitable example.</p>	
Q4	(10 marks)	
a)	<p>Differentiate between Thevenin's and Norton's theorems with suitable circuit diagrams and equations.</p>	
OR		
b)	<p>Calculate current in 10 ohm branch using thevenin's theorem.</p>	
		
Q5	(10 marks)	
a)	<p>What is power? Define Active, Reactive and Apparent Power with power triangle.</p>	
OR		
b)	<p>An alternating voltage is given by <math>V = 230 \sin 314t</math>. Calculate  a) Frequency b) Maximum value c) Average value d) RMS value</p>	

CO1

CO2