

H

Roll No.

TEE-201

**B. TECH. (SECOND SEMESTER)
END SEMESTER EXAMINATION, 2018**

(All Branches)

BASIC ELECTRICAL ENGINEERING

Time : Three Hours

Maximum Marks : 100

Note : (i) This question paper contains five questions with alternative choice.

(ii) All questions are compulsory.


(iii) Instructions on how to attempt a question are mentioned against it.

(iv) Each part carries ten marks. Total marks assigned to each question are twenty.

1. Attempt any *two* questions of choice from (a), (b) and (c). $(2 \times 10 = 20 \text{ Marks})$

(a) State KCL, Node, Mesh and Ohm's law.

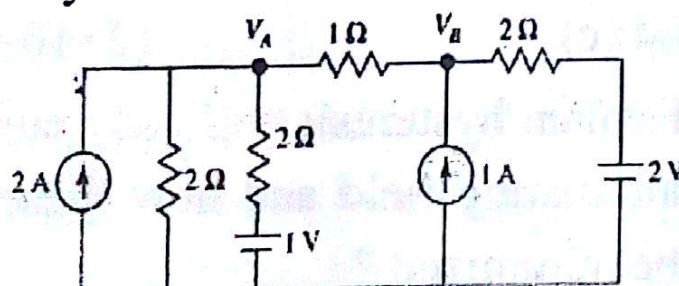(b) Calculate nodal voltage at A and B in the circuit shown in Fig. by using nodal analysis.



(2)

TEE-201

- (c) A particular load is to be driven at about 900 r.p.m. What should be the number of poles for a 3- ϕ induction motor when (i) $f = 50$ Hz, (ii) $f = 60$ Hz? Calculate the actual speed in each case if the rated slip is 6%.
2. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Explain principle and construction of D. C. motor with suitable diagram. Derive an expression for back EMF.
- (b) A series RLC circuit with $R = 12$ ohms, $L = 1$ mH and $C = 10$ mF has an applied voltage of 220 V at which current maximum in the series circuit. Calculate the resonating frequency, current in the circuit and quality factor of the circuit.
- (c) Draw magnetic circuit with expression for m.m.f. in the circuit. Also write analogy between electrical and magnetic circuit.
3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Explain hysteresis and eddy current loss in alternating field and how these losses can be minimized?

F. No. a-80

(3)

TEE-201

- (b) The readings on two wattmeter's connected to measure three-phases power in star connected load are 12.0 kW and 6.0 kW respectively with phase current 10 A in each phases. Calculate the power factor, active power, line voltage and phase voltage.
- (c) Derive an expression for three-phase total power on balanced load measured by two wattmeter method.
4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Define the following :
- Frequency
 - Form Factor
 - Quality Factor
 - Time period
 - Phase
- (b) A 5 kVA, 250/500 V, 50 Hz, single-phase transformer gives the following test results :
- No-load : 250 V 0.75 A 60 W
(LV side)
- Short Circuit test : 9 V 6 A 21.6 W
(HV side)

F. No. : a-80

P. T. O.

(4)

TEE-201

Calculate :


- (i) What are the values of core loss component I_c and magnetizing component I_m across core of the transformer?
 - (ii) Find the value of x (load factor) for which maximum efficiency obtained. Calculate the maximum efficiency at .8 lagging p. f.
 - (c) What is meant by O. C. and S. C. test in single-phase transformer? Explain with the help of equivalent circuits and mathematical expression.
5. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Is three-phase induction motor is self start or not? Explain the concept of three-phase rotating magnetic field.
 - (b) A d.c. shunt machine connected to 200 V supply has resistance of armature as 1 ohm and of field winding as 80 ohm. Find the value of e.m.f. (E) if it design as a generator and for as a motor.

F. No. : a-80

(5)

TEE-201

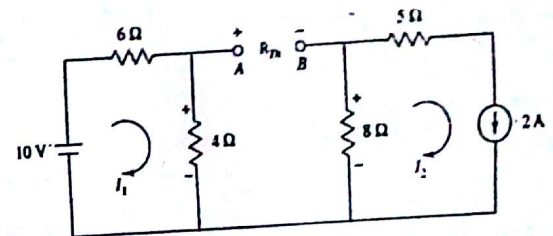- (c) State Norton's theorem d.c. circuit with its equivalent diagram and determine $R_N = R_{Th}$ across the A and B terminal for given circuit.



TEE-201

410

F. No. : a-80