

TEE-201**B. TECH. (SECOND SEMESTER)
END SEMESTER EXAMINATION, 2019****(ALL BRANCHES)****BASIC ELECTRICAL ENGINEERING****Time : Three Hours****Maximum Marks : 100**

Note : (i) This question paper contains five questions.


(ii) All questions are compulsory.

(iii) Instructions on how to attempt a question are mentioned against it.

(iv) Total marks assigned to each question are twenty.

1. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

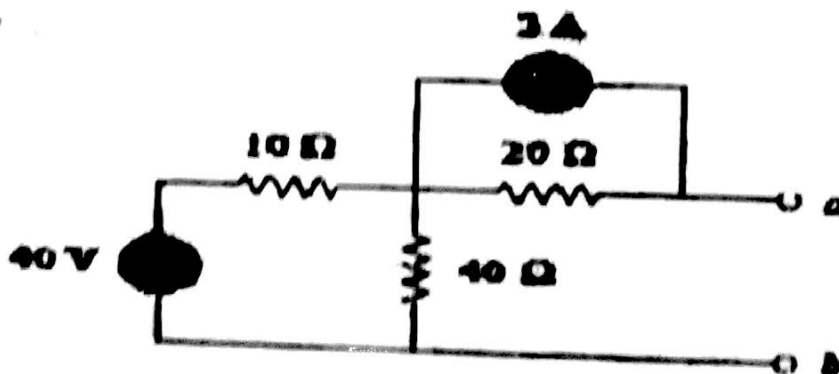(a) Find the Thevenin's equivalent at terminal *a-b* of the circuit :



(2)

TEE-201

- (b) Describe about independent and dependent energy sources.
- (c) State and explain the superposition theorem. Illustrate the application of this theorem with reference to an appropriate circuit.
2. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Describe the resonance condition in series RLC circuit and draw phasor diagram to illustrate relation between V and I in series RLC circuit.
- (b) A circuit consist of two coils in series connected to a 200 V a.c. supply. The first coil has a resistance of 5 ohm and inductive reactance of 10 ohm. The second coil has a resistance of 6 ohm and inductive reactance of 8 ohm.
- Calculate :
- (i) total impedance of the circuit, (ii) the current flowing in circuit, (iii) circuit phase angle, (iv) voltage drop in each coil.
- (c) Derive the relationship between line and phase quantities for star and delta connections.

F. No. : b-49

(3)

TEE-201

3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Explain in detail, different types of losses accruing in single-phase transformer.
- (b) In a 25 kVA, 2000 V/ 200 V transformer the iron and copper losses are 200 W and 400 W respectively. Calculate the efficiency at half-load and 0.8 power factor lagging. Also determine the maximum efficiency and corresponding load.
- (c) Explain the working of single-phase transformer. Also derive its EMF equation.
4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Why is earthing essential ? Explain its advantages.
- (b) Write short notes on MCBs & ELCBs.
- (c) Why is power factor correction necessary ? Describe any *one* method with circuit diagram.
5. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Draw and explain characteristics of series and shunt D.C motors.

F. No. : b-49

P. T. O.

- (b) A 250 V d. c. shunt motor takes 30 A current while running at full-load. The resistance of motor armature and field windings are 0.1Ω and 200Ω respectively. Determine :
- (i) shunt field current
 - (ii) armature current
- (c) Explain the working of three-phase Induction motor.