

(6)

TEE-201

- (iii) The frequency of induced EMF in rotor
- (iv) Speed of rotor mmf relative to rotor winding.
- (c) Write short notes on the following : (CO4)
- (i) Batteries
 - (ii) DC motor
 - (iii) Induction motor
 - (iv) Types of Switches.

TEE-201

1,550

H

Roll No.

TEE-201

**B. TECH. (SECOND SEMESTER)
END SEMESTER**


EXAMINATION, June, 2023

BASIC ELECTRICAL ENGINEERING

Time : Three Hours

Maximum Marks : 100

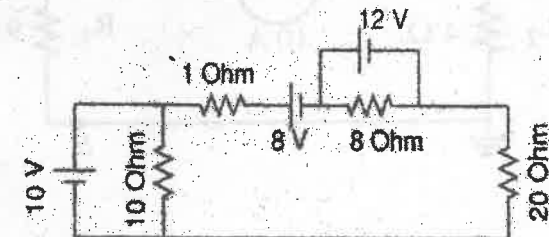- Note :** (i) All questions are compulsory.
- (ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.
- (iii) Total marks in each main question are **twenty**.
- (iv) Each sub-question carries 10 marks.
1. (a) Find the current through superposition theorem in 20 Ohm. (CO1)




P. T. O.


(2)

TEE-201

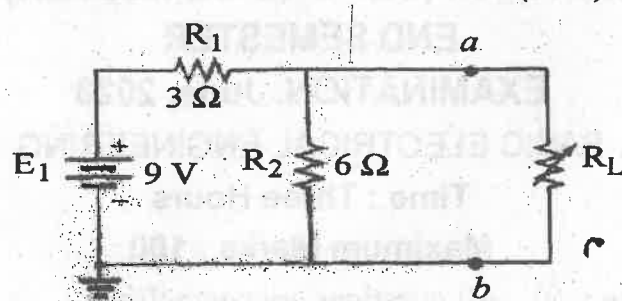- (b) Find the Thevenin equivalent circuit for the network in the shaded area of the network given. Then find the current through R_L for value of 2, 10 and 100 Ohm. (CO1)



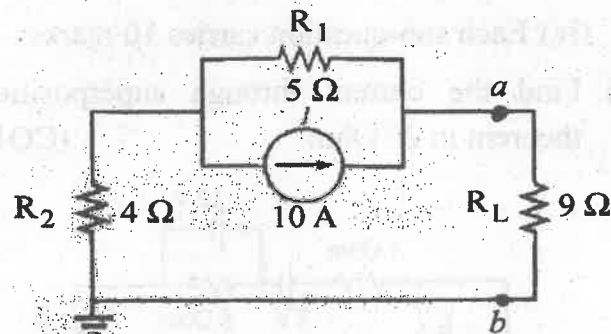
- (c) Find the Norton equivalent circuit for the load resistance of 9-Ohm in Fig. (CO1)



(3)

TEE-201

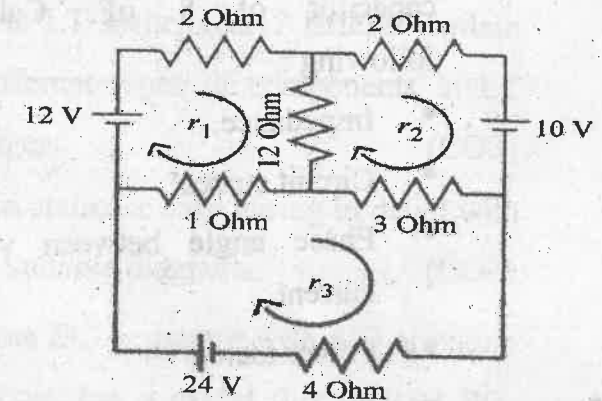2. (a) By using Kirchhoff's voltage law (KVL)/Mesh analysis find the current flowing through a 4 Ohm resistor. (CO2)



- (b) Find the impedance of a series RLC circuit if the inductive reactance, capacitive reactance, and resistance are 184 Ohm, 144 Ohm and 30 Ohm respectively. Also calculate the phase angle between voltage and current. (CO2)

- (c) Define the following : (CO2)

- * Q-factor
- * Resonance in series R-L-C circuit
- * RMS and Average values
- * Form factor and Peak factor

P. T. O.

(4)

TEE-201

3. (a) A 240 V, 50 Hz AC supply is applied to a coil of 0.08 H inductance and 4Ω resistance connected in series with a capacitor of $8 \mu\text{F}$. Calculate the following : (CO2)

- * Impedance,
- * Circuit current,
- * Phase angle between voltage and current,
- * Power factor,
- * Power consumed,
- * Q-factor of the circuit at resonant frequency.

- (b) A resistor R in series with a capacitor C is connected to a 50 Hz, 240 V supply. Find the value of C so that R absorbs 300 W at 100 V. Also find the maximum charge and the maximum stored energy in C. (CO2)

- (c) The equation for an alternating current is given by $i = 77 \sin 314t$. Find the peak value, frequency, time period and instantaneous value at $t = 2 \text{ ms}$. (CO2)

(5)

TEE-201

4. (a) Explain MCCB with a suitable diagram. Also write the main differences between MCB and MCCB. (CO3)
- (b) What is LT switchgear ? Briefly explain the different types of components in LT switchgear. (CO3)
- (c) Explain staircase case wiring in detail with all the suitable diagrams. (CO3)
5. (a) A 4 pole DC generator with 400 armature conductors has a useful flux of 0.04 Wb. What is the emf induced if the machine is wave wound and runs at 1200 rpm ? What must be the speed at which the machine should be driven to generate the same emf if the machine is lap wound. (CO4)
- (b) A three phase 50 Hz, 6-pole induction motor is running with a slip of 3%. Calculate : (CO4)
- (i) The speed of the rotating field
 - (ii) The motor speed

P. T. O.