

ROLL NO.

--	--	--	--	--	--	--	--

PAPER CODE: TEE 101

B.TECH
MID SEMESTER EXAMINATION, 2018
(I SEMESTER)
BASIC ELECTRICAL ENGG

Time: 1:30 Hours

MM: 50

Note:

1. This question paper contains two sections.
2. Both Sections are compulsory.

SECTION - A

1. Fill in the blanks/True- False.

(1x5=5 Marks)

a Independent sources are of four types named as

b During resonance in series RLC circuit power factor will be zero value (T/F)

c In series RLC circuit power factor is leading that means Value of $X_C > X_L$ (T/F)

d Six light bulbs are connected in parallel across 110 V. Each bulb is rated at 75 W. The current flows through each bulb is.....

e In a series RLC circuit if quality factor Q is increased by twice then bandwidth is also increased twice (T/F)

2. Attempt any five.

(3x5=15 Marks)

a State and explain Ohm's law. Give its limitations.

b What is mean by Active and Passive elements .?

c Define KCL and KVL for a circuit.

d Draw the resonance graphical curve for different values of frequency


e Define average value and rms value.

f Define bandwidth in series RLC circuit.

Each question contains three parts a, b and c. Attempt any two parts of choice from each question.

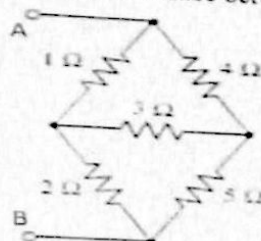3. (5x2=10 Marks)

- State the statement of Superposition theorem and Norton's theorem.
- For the below given circuit find equivalent resistance between A & B.




- Derive the expression for voltage and current in series RL circuit with phasor diagram.

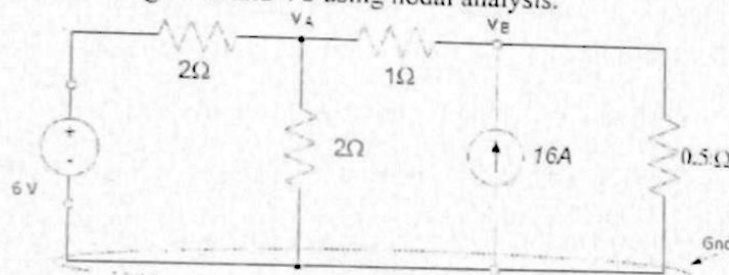4.

(5x2=10 Marks)

- Define frequency, time period, quality factor and unilateral elements.
- Find the value nodal voltages V_a and V_b using nodal analysis.



- Derive the relation for three phase star connection phase voltage and line voltage

5. (5x2=10 Marks)

- Explain Thevenin's theorem with an example.

b.

A coil of 2Ω resistance and 0.01 H inductance is connected in series with a capacitor across 230 V mains. What must be the capacitance, in order that maximum current occurs at a frequency of 50 Hz ? Find also the current and the voltage across the capacitor.

- For given circuit shown below find load current for resistance $R_L = 5 \text{ ohm}$.

