

TEC-201

B. TECH. (SECOND SEMESTER) END SEMESTER EXAMINATION, 2019 (ALL BRANCHES)

BASIC ELECTRONICS ENGINEERING

Time : Three Hours

Maximum Marks : 100

Note : (i) This question paper contains five questions.

(ii) All questions are compulsory.

(iii) Instructions on how to attempt a question are mentioned against it.

(iv) Total marks assigned to each question are twenty.

1. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Discuss laws of Boolean algebra in detail.

(b) Perform the following number system conversion :

(i) $(43)_{10} = (?)_2$

(ii) $(59)_{10} = (?)_{BCD}$

(iii) $(13)_8 = (?)_2$

(iv) $(11011001)_2 = (?)_{16}$

(v) $(AC)_{16} = (?)_{10}$

(2)

TEC-201


- (c) Perform the following :
- $(38)_{10} - (25)_{10}$ in Binary using 1's complement
 - $(29)_{10} - (34)_{10}$ in Binary using 2's complement
2. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- Derive the continuity equation for semiconductors.
 - Differentiate between insulators, semiconductors and conductors in detail.
 - Write short notes on the following :
 - P type semiconductors
 - Current density
3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- What do you mean by the depletion layer of a PN junction diode ? Compare V-I characteristics of Silicon and Germanium diodes.
 - Discuss the working of a center tapped full wave rectifier and derive its rectification efficiency.
 - The reverse saturation current at 300 K of a *p-n* junction Ge diode is $5 \mu\text{A}$. Find voltage to be applied across the diode to obtain a forward current of 8 mA. Also determine its static and dynamic resistance.

F. No. : b-38

(3)

TEC-201

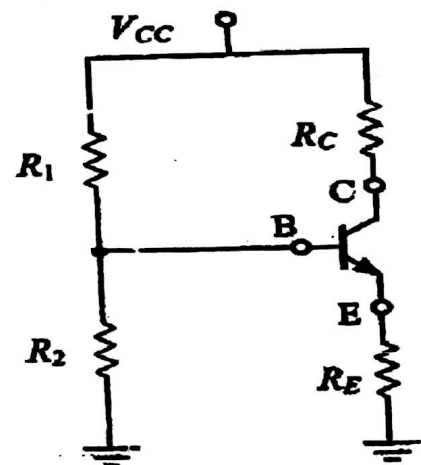4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- Derive the mathematical relation between current gains α and β of a BJT. Also discuss the leakage currents I_{CBO} and I_{CEO} .
 - Discuss the construction, operation and characteristics of E-MOSFET.
 - Consider the following voltage divider bias circuit of BJT. Determine the collector current I_C and collector to emitter voltage V_{CE} . Given, $R_1 = 60 \text{ k}\Omega$, $R_2 = 7 \text{ k}\Omega$, $R_C = 12 \text{ k}\Omega$, $R_E = 1.7 \text{ k}\Omega$, $V_{BE} = 0.7 \text{ V}$, current gain $\beta = 50$ and $V_{CC} = 30 \text{ V}$.



F. No. : b-38

P. T. O.

5. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Write characteristics of an ideal Op-Amp. Also discuss the concept of virtual ground.

(b) Draw neat circuit diagrams and derive the output of the following Op-Amp based circuits :

(i) Adder

(ii) Subtractor

(c) What do you mean by an inverting amplifier ? Discuss, how an Op-Amp can be used as a differentiator ?