

(4)

TEE-101

5. (a) Define Active, Reactive and Apparent Power. Also give significance of power factor. (CO2)

OR

- (b) Derive the relation between line and phase quantity for delta connection with the help of phasor diagram. (CO2)

TEE-101

2,020

H

Roll No.

TEE-101

B. TECH. (FIRST SEMESTER)
MID SEMESTER EXAMINATION, 2021-22

(All Branches)

BASIC ELECTRICAL ENGINEERING


Time : 1 : 30 Hours

Maximum Marks : 50

Note : (i) Answer all the questions by choosing any *one* of the sub-questions.

(ii) Each question carries 10 marks.

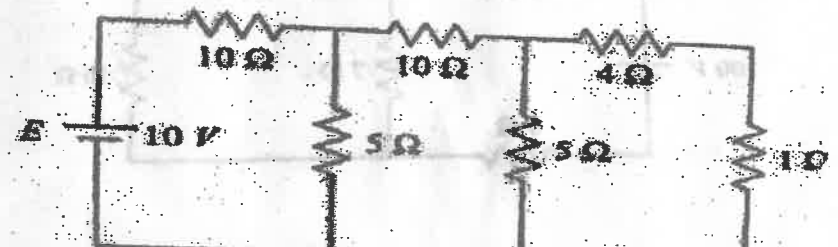1. (a) Calculate branch currents using mesh analysis. (CO1)



(2)


TEE-101

OR

- (b) Calculate current across load branch 5 ohm using Thevenin's theorem. (CO1)




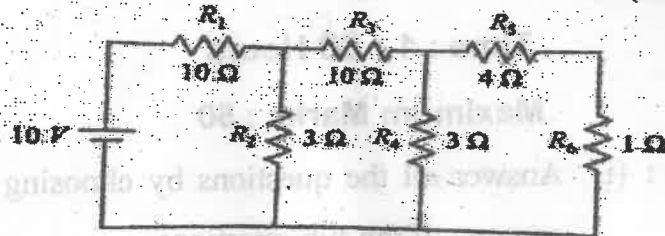2. (a) Calculate current across each resistor using Nodal Analysis. (CO1)



OR

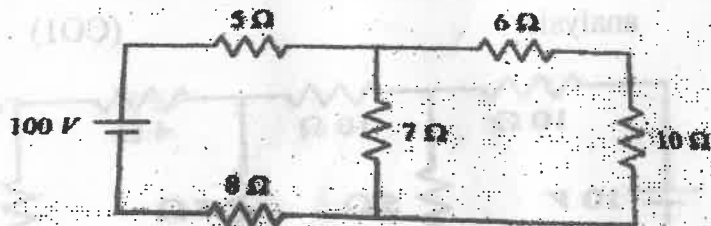- (b) Calculate current in load branch 10 ohm using Norton's Theorem. (CO1)



(3)

TEE-101

3. (a) Derive expression for RMS and Average Value for Half Wave AC. (CO2)

OR

- (b) Draw the circuit diagram and give expression for RL, RC and RLC series circuit. (CO2)

4. (a) Define the following :

- (i) Kirchhoff's current law
- (ii) Active elements
- (iii) Linear elements
- (iv) Bilateral elements
- (v) Kirchhoff's voltage law for DC circuit. (CO1, CO2)

OR

- (b) Explain condition for resonance in a RLC series circuit. Derive the expression for resonant frequency. (CO1, CO2)