

TEE-101**B. TECH. (FIRST SEMESTER)
MID SEMESTER EXAMINATION, 2018****(All Branches)****BASIC ELECTRICAL ENGINEERING****Time : 1:30 Hours****Maximum Marks : 50**

Note : (i) This question paper contains two Sections.

(ii) Both Sections are compulsory.

Section—A

1. Fill in the blanks/True/False : (1×5=5 Marks)
 - (a) Ohm's law characteristics linear for R and non-linear for L and C. (True/False)
 - (b) In an RLC series circuit at resonance current is maximum. (True/False)
 - (c) Line Voltage lead by an angle from phase voltage in three phase star connection.
 - (d) Quality factor value changes when change in frequency observes in series RLC circuit. (True/False)

(2)

TEE-101

- (e) In a.c. circuit power consumed by R in terms of, inductor and capacitor consume in terms of

2. Attempt any *five* parts : (3×5=15 Marks)

- What is node and mesh in a circuit ? Draw an circuit having all nodes and mesh.
- What is meant by ideal and practical voltage source ?
- Define resonance and draw the phasor diagram with complete graphical representation during resonance.
- Why is three phase advantageous than single phase a.c. circuit ?
- Define frequency, time-period and form factor of sinusoidal waveform.
- Define superposition theorem.

Section—B

3. Attempt any *two* parts of choice from (a), (b) and (c). (5×2=10 Marks)


- State Thevenin's theorem with complete equivalent circuit. Why is it useful in electrical circuits ?

F. No. : b-45

(3)

TEE-101

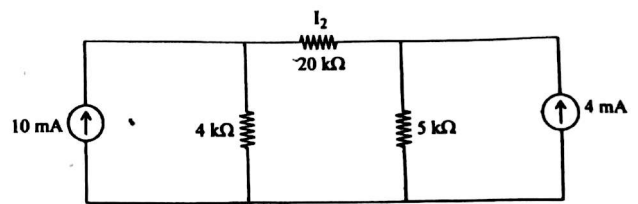- (b) Using the method of superposition, calculate the branch current I_2 in the circuit shown in Figure :



- Derive the expression form phasor relationship between line voltage and phase voltage, line current and phase current in three-phase delta circuit.
4. Attempt any *two* parts of choice from (a), (b) and (c). (5×2=10 Marks)
- Explain the following with suitable examples and/or circuit diagram(s) :
 - Quality factor
 - RMS and Average value
 - Unilateral and Bilateral elements
 - Independent sources
 - A 100 V, 50 Hz supply is applied across the series circuit consisting of $R = 10\Omega$, $L = 1\text{ mH}$ and $C = 20\text{ }\mu\text{F}$. Find the input current and voltage across each element.

F. No. : b-45

P. T. O.

- (c) Derive the expression for Bandwidth in series a.c. circuit.
5. Attempt any *two* parts of choice from (a), (b) and (c). (5×2=10 Marks)
- (a) Derive the expression for Delta to Star conversion in resistive d.c. network.
- (b) A coil having a resistance of $5\ \Omega$ and an inductance of 0.2 H is connected in series with a $40\text{-}\mu\text{F}$ capacitor. The voltage applied to the circuit is 220 V . Determine the maximum current and corresponding frequency. Also, find the voltage across the capacitor and coil for this frequency.
- (c) Consider the circuit shown in figure and determine Thevenin equivalent circuit for the load resistance R_L . Then determine I_L if R_L is $4, 8$ and $10\text{ k}\Omega$.

