

H

Roll No. ....

## TCS-301

### B. TECH. (THIRD SEMESTER) END SEMESTER

EXAMINATION, Jan., 2023

LOGIC DESIGN

Time : Three Hours

Maximum Marks : 100

- Note :
- (i) All questions are compulsory.
  - (ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.
  - (iii) Total marks in each main question are **twenty**.
  - (iv) Each sub-question carries 10 marks.

1. (a) (i) Prove that : (CO1)  
$$(AB + CD) = ((AB)'.(CD)')'$$
  
(ii)  $(A + B).(C + D) = ((A + B)' + (C + D)')'$  with the fact that AND-OR configuration is equivalent to NAND-NAND and OR-AND configuration is equivalent to NOR-NOR configuration.  $3+3=6$

P. T. O.

- (b) Simplify using K-map. (CO1)

$$f(A, B, C, D, E, F) = \pi M(4, 5, 6, 7, 8, 12, 13, 16, 17, 18, 19, 21, 22, 25, 28, 32, 35, 37, 38, 39, 40, 53).$$

7

- (c) Simplify the following by finding the essential prime implicants : (CO1)

$$f(A, B, C, D) = \Sigma(1, 3, 4, 5, 10, 11, 12, 13, 14, 15).$$

7

2. (a) Design a 3-bit majority circuit which gives output '1' when input variables have more number of '1's than '0's. (CO2)

- (b) Construct 5 to 32 line decoder using 3 to 8 decoder and 2 to 4 decoder as enable circuits. (CO2)

- (c) Realize circuit  $f(A, B, C, D) = \Sigma(0, 2, 5, 7, 11, 14)$  using 8 : 1 mux with D as control variable. (CO2)

- (d) Design combinational circuits : (CO2)

$$F1(A, B, C) = \Sigma(3, 5, 6)$$

$$F2(A, B, C) = \Sigma(1, 4)$$

$$F3(A, B, C) = \Sigma(2, 3, 5, 6, 7) \text{ using decoder and NAND gates.}$$


4×5=20

3. (a) Realized JK flip-flop and T Flip-flop from D-flip-flop. Draw the relevant diagram for conversion and deduce the characteristics equation. 8 (CO3)
- (b) A sequential circuit has two JK flip-flops, two inputs x and y and one output Z. Draw the logic diagram (Circuit diagram). Deduce the state table and state diagram. 8 (CO3)

$$J_A = Bx + \bar{B}y : K_A = \bar{B}x\bar{y}, J_B = \bar{A}x$$

$$K_B = A = x\bar{y}, Z = A\bar{x}\bar{y} + B\bar{x}\bar{y}.$$

 4. (a) Reduce that state transition diagram by row elimination method and implication table method. Deduce the output of the new states for the input string 0110110101110. 10 (CO3)



- (b) How data 01101001 is transferred through SIPO with suitable circuit diagram realized with JK flip-flop. How the circuit gets modified if the data transferred in SISO and PIPO configuration. 10 (CO4)
5. (a) Design synchronous 4-bit Up/Down Counter using JK flip-flop. 6 (CO5)
- (b) Design mod 6 counter using T flip-flop. 6 (CO5)
- (c) Design asynchronous sequential logic circuit that has 2 inputs A & B, one output 'x'. Output goes high when A = 1 and B makes transition from 1 to 0. X remains high as this A = 1 and B = 0. It becomes '1' when A = 1 and B goes from 1 to 0. Draw the state transition diagram, state reduction table, modified state diagram and circuit diagram. 8 (CO5)