

(4)

TEE-201

- (c) Define Batteries, type and characteristics of batteries, also differentiate between primary and secondary batteries. (CO4)
5. (a) A 4 pole DC generator has 51 slots and each slot contains 20 conductors. The machine has a useful flux of 0.007 Wb and its speed is 1500 RPM. Find the induced EMF if the machine is (i) Lap connected (ii) Wave connected. (CO5)
- (b) Explain working of three phase induction motor and also given necessary condition to generate rotating magnetic field. (CO5)
- (c) Explain working principle of DC motor along with its EMF equation. (CO5)

TEE-201

1,100

H

Roll No.

TEE-201

**B. TECH. (SECOND SEMESTER)
END SEMESTER**

EXAMINATION, July/August, 2022

BASIC ELECTRICAL ENGINEERING

Time : Three Hours

Maximum Marks : 100

Note : (i) All questions are compulsory.

(ii) Answer any *two* sub-questions among (a), (b) and (c) in each main question.

(iii) Total marks in each main question are **twenty**.

(iv) Each sub-question carries 10 marks.


1. (a) Differentiate between Thevenin and Norton theorem with an example. (CO1)

P. T. O.


(2)

TEE-201

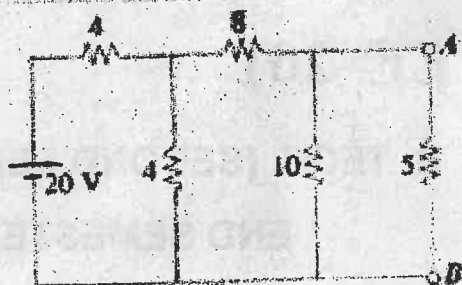- (b) Calculate current across 5 ohm using Norton theorem : (CO1)



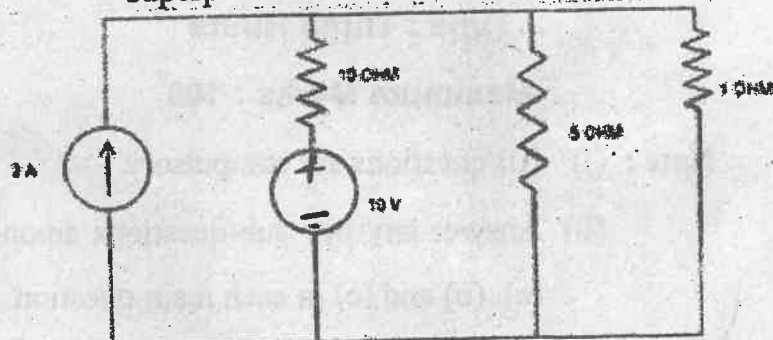- (c) Calculate current across 1 ohm using superposition theorem : (CO1)



2. (a) Derive the relation between line and phase quantities for three phase AC circuits for star and delta connection. (CO2)
- (b) Explain the significance of power factor. Also discuss any *one* technique for its improvement. (CO2)

(3)

TEE-201

- (c) Draw the phasor diagram of a series RLC circuit energized by a sinusoidal voltage showing the relative position of the current, voltage and applied voltage for the following cases : (CO2)

(i) when $X_L > X_C$

(ii) when $X_L < X_C$

(iii) when $X_L = X_C$

3. (a) Draw and explain the equivalent circuit of a transformer on load. (CO3)
- (b) What is auto-transformer ? Discuss its working, application, advantages and disadvantages. (CO3)
- (c) Explain the working of transformer (i) at no load condition (ii) at full load condition along with proper circuit diagram. (CO3)
4. (a) Differentiate between MCB and MCCB. (CO4)
- (b) Describe components of LT switchgear in detail. (CO4)

P. T. O.