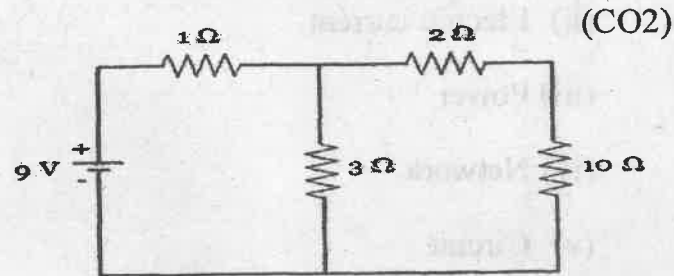


(4)

TEE-201

- (ii) For the given circuit, determine the current flowing through $10\ \Omega$ Resistor using Norton's theorem.



(CO2)

OR

- (b) Find current in $1\ \Omega$ resistance using nodal analysis.

(CO2)



5. (a) What is power? Define Active, Reactive and Apparent Power with Power triangle.

(CO2)

OR

- (b) Derive the RMS and Average values of a single-phase AC.

(CO2)

TEE-201

1,550

H

Roll No.

TEE-201

B. TECH. (SECOND SEMESTER)

MID SEMESTER

EXAMINATION, April, 2023

BASIC ELECTRICAL ENGINEERING


Time : $1\frac{1}{2}$ Hours

Maximum Marks : 50

Note : (i) Answer all the questions by choosing any *one* of the sub-questions.

(ii) Each sub-question carries 10 marks.

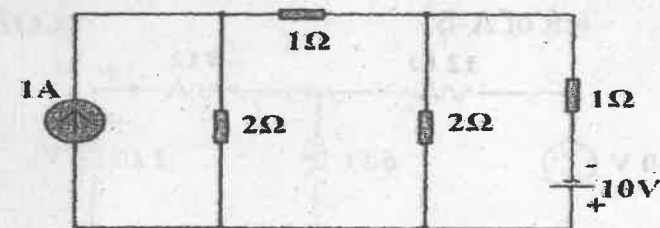1. (a) Using mesh analysis, obtain the current through the $10\ \text{V}$ battery for the circuit shown in figure : (CO2)




P. T. O.

(2)


TEE-201

OR

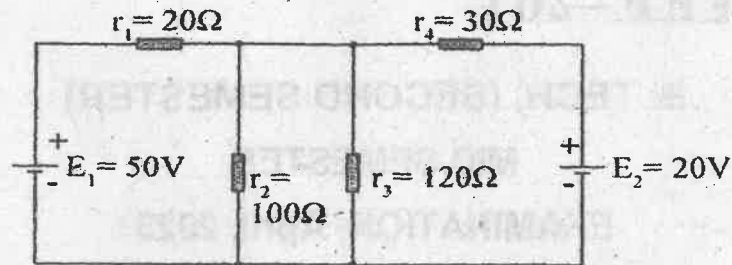- (b) Calculate current in r_2 using nodal analysis. (CO2)




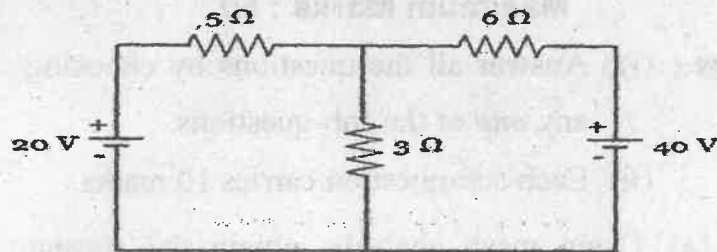2. (a) Calculate current in 3-ohm resistor using superposition theorem. (CO2)



OR

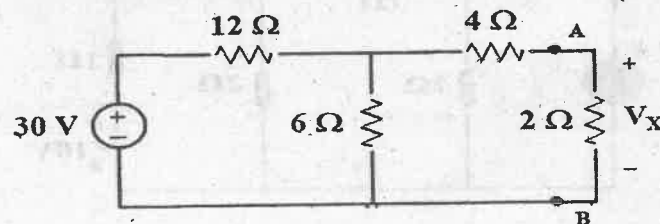- (b) Find V_x by first finding V_{TH} and R_{TH} to the left of A-B. (CO2)



(3)

TEE-201

3. (a) Define the following: (CO1)

- (i) Charge
- (ii) Electric current
- (iii) Power
- (iv) Network
- (v) Circuit

OR

- (b) (i) Explain Kirchhoff's Law with example.

- (ii) A $20\ \Omega$ resistor is connected in parallel with a $60\ \Omega$ resistor. If the combination is connected across a 30 volts battery supply, find the current flowing through each resistor and the total current supplied by the source. (CO1)

4. (a) (i) Differentiate between Thevenin's and Norton's theorem.

P. T. O.