

H

Roll No.

TEC-201

B. TECH. (SECOND SEMESTER) END SEMESTER EXAMINATION, 2018

(All Branches)

BASIC ELECTRONICS ENGINEERING

Time : Three Hours

Maximum Marks : 100

Note : (i) This question paper contains five questions with alternative choice.

(ii) All questions are compulsory.

(iii) Instructions on how to attempt a question are mentioned against it.

(iv) Each part carries ten marks. Total marks assigned to each question are twenty.

1. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) (i) What are universal gates ? Realize AND, OR and EX-OR gates using NAND gates only.

(ii) State De-Morgan's theorem. Apply De-Morgan's theorem and simplify the following :

$$Y = \overline{\overline{A + BC} + D(E + \overline{F})}$$

(2)

TEC-201

- (b) (i) Convert the following numbers as indicated :

(1) $(4021.25)_{10} = ()_2$;

(2) $(A6F.CD)_{16} = ()_8$

- (ii) Minimize the following functions using Boolean algebra rules :

(1) $Y = AB + A(B + C) + B(B + C)$

(2) $Y = A + AB + ABC + ABCD + \dots$

- (c) (i) Perform BCD addition of $(184)_{10}$ and $(576)_{10}$.

- (ii) Subtract the following :

(1) $(1011)_2 - (1100)_2 = \dots$ with the help of 2's complement.

(2) $(10110)_2 - (10011)_2 = \dots$ with the help of 1's complement.

2. Attempt any two questions of choice from (a), (b) and (c). (2×10=20 Marks)

- (a) (i) Distinguish between intrinsic semiconductor and extrinsic semiconductor. What happens to the conductivity of a semiconductor with the rise in temperature ?

- (ii) What is meant by Fermi level in a semiconductor ? Describe Fermi level in context of intrinsic and extrinsic semiconductors.

(3)

TEC-201

- (b) (i) State and discuss mass action law.

- (ii) What is the concentration of holes in silicon crystals having donor concentration of $1.4 \times 10^{24}/\text{m}^3$? Intrinsic carrier concentration is $1.4 \times 10^{18}/\text{m}^3$. Find the ratio of electron to hole concentration.

- (c) (i) Define diffusion and drift currents in a semiconductor.

- (ii) Free electrons and holes mobilities for pure silicon and pure germanium are given as follows :

For pure germanium

$$\mu_e = 3800 \text{ cm}^2/\text{V-s},$$

$$\mu_h = 1800 \text{ cm}^2/\text{V-s}$$

For pure silicon $\mu_e = 1300 \text{ cm}^2/\text{V-s},$

$$\mu_h = 500 \text{ cm}^2/\text{V-s}$$

Determine the values of intrinsic conductivity for both.

Assume intrinsic concentration $n_i = 2.5 \times 10^{13} \text{ cm}^{-3}$ for germanium and $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ for silicon at room temperature.

P. T. O.


(4)

TEC-201

3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Draw the forward and reverse characteristics of a $p-n$ junction diode. State the relationship in between forward current and forward voltage. Explain Zener and Avalanche breakdown mechanisms in reverse bias diode.

(b) Sketch i_R and V_o for the circuit :

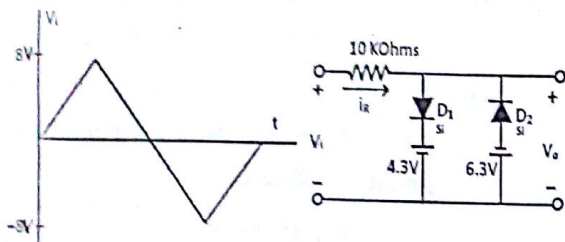

(c) Draw the circuit and discuss the working of full wave bridge rectifier using suitable input and output waveform.

4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Draw and explain input and output characteristics of common emitter configuration (CE) using NPN BJT. Indicate all the regions of operation.

F No. : a-80

(5)


TEC-201

- (b) Why is transistor biasing required ? Determine the following for the BJT bias circuit shown in the figure given below. Assume Si-BJT. Given that $\beta = 80$:

(i) Type of biasing

(ii) I_C

(iii) V_{CE}

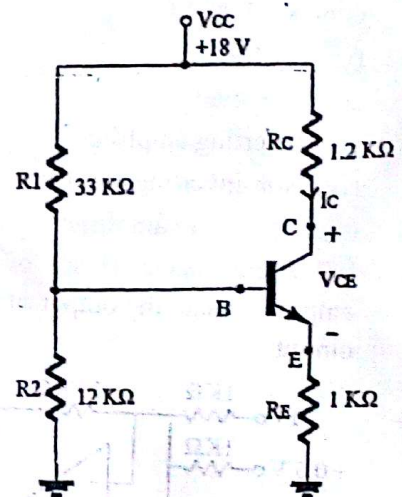

- (c) Differentiate in between unipolar and bipolar semiconductor devices by giving *two* examples of each. Draw the structure of JFET and explain its principle of operation.

F. No. : a-80

P. T. O.

5. Attempt any *two* questions of choice from (a), (b) and (c). $(2 \times 10 = 20 \text{ Marks})$

(a) Describe the concept of virtual ground in op-amp. circuits. Draw the circuit diagram of an integrator using op-amp. and explain its working.

(b) Write short notes on the following in context of op-amps. :

- (i) CMRR
- (ii) Slew rate
- (iii) Inverting amplifier
- (iv) Non-inverting amplifier
- (v) Unity gain amplifier

(c) Enlist the characteristics of an ideal op-amp. Calculate the output of the following circuit :

