

**TEE-101****B. TECH. (FIRST SEMESTER)  
END SEMESTER EXAMINATION, 2018  
(ALL BRANCHES)****BASIC ELECTRICAL ENGINEERING****Time : Three Hours****Maximum Marks : 100**

**Note :** (i) This question paper contains five questions with alternative choice.


(ii) All questions are compulsory.

(iii) Instructions on how to attempt a question are mentioned against it.

(iv) Each part carries ten marks. Total marks assigned to each question are twenty.

1. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

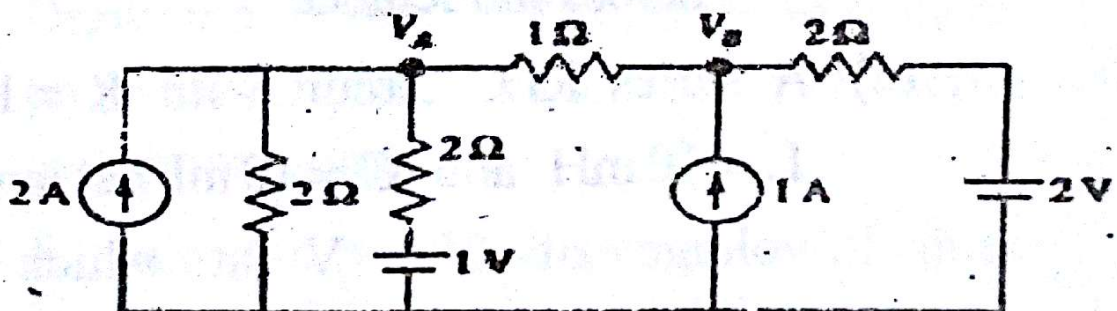(a) Use Nodal Analysis to find out current in 1 ohm resistor.



(2)

TEE-101

- (b) State and explain Norton's theorem with suitable example.
- (c) Write short notes on :
- (i) Dependent and Independent energy sources.
  - (ii) Current division rule and voltage division rule.
  - (iii) Unilateral and bilateral elements.
  - (iv) Active and passive elements.
2. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Why is ac more advantageous than dc and explain with circuit diagram current behavior in R, L, C, R-L and R-C circuits.
- (b) An inductance of 0.5 H in series with resistor  $10\Omega$ . The circuit connected across 220V, 50Hz single phase AC supply. Find the following in circuit :
- (i) Current
  - (ii) Voltage across resistor and voltage across inductance
- (c) A series RLC circuit with  $R = 10\text{ ohms}$ ,  $L = 10\text{mH}$  and  $C = 10\text{mF}$  has an applied voltage of 200 V at which current maximum in the series circuit. Calculate

(3)

TEE-101

- the resonating frequency, current in the circuit and quality factor and bandwidth of the circuit.
3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Explain in detail construction and working of single phase transformer.
- (b) What are the different types of losses that occur in single phase transformer ? How can we minimize them ?
- (c) A 2200/220 V, 100 kVA, 50 Hz single phase transformer gave the following test results :
- OC Test : 2000 V, 4.5 A, 2 kW
- SC Test : 22 V, 9.09 A, 3 kW
- Determine the efficiency of transformer at full load for 0.9 pf lagging.
4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Draw and explain with applications based on speed-torque characteristic of DC series and shunt motor.
- (b) Explain the working principle of three phase induction motor in detail.

(c) A 250 V dc shunt motor takes 30 A current while running at full load. The resistance of motor armature and field windings are  $0.1 \Omega$  and  $200 \Omega$  respectively. Determine :

- (i) Shunt field current
- (ii) Armature current
- (iii) Back e.m.f. generated in the motor, when it runs on full load.

5. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Write short notes on the following :

MCB, ELCB and MCCB

(b) Explain the following :

- (i) Power factor
- (ii) Methods of Power factor correction with circuit diagram

(c) A balanced star-connected load of  $(8 + j6)\Omega$  per phase is connected to a balanced 3-phase, 440 V supply :

Find the :

- (i) Line current
- (ii) Power factor
- (iii) Active power