

H

Roll No. ....

**TMC-102**

**M. C. A. (FIRST SEMESTER)**

**MID SEMESTER**

**EXAMINATION, Nov., 2022**

**COMPUTER ORGANIZATION AND  
ARCHITECTURE**

**Time : 1½ Hours**

**Maximum Marks : 50**

**Note :** (i) Answer all the questions by choosing  
any *one* of the sub-questions.

(ii) Each sub-question carries 10 marks.

1. (a) Define the importance of logic gate in digital circuits. Explain any *four* logic gates with diagram, working, and truth table. (CO1)

**P. T. O.**

(2)

TMC-102

OR

- (b) How information is represented in a computer ? Define computer hardware generation. (CO1)
2. (a) Write a short note on K-Map. In which situation K-Map is not useful ? Clarify the following with respect to K-Map : (CO2)
- (i) Pair
  - (ii) Quad
  - (iii) Octet
  - (iv) Rolling
  - (v) Overlapping

OR

- (b) In your opinion, which circuit is useful for adding 3 binary digits ? Explain the related circuit diagram with its truth table and working. Explain half subtractor. (CO2)
3. (a) What do you mean multiplexer and encoder ? Explain  $4 \times 1$  Mux and Octal to Binary encoder. (CO1)

(3)

OR

- (b) Write a short note on Von Neumann Machine and Register Transfer Language. (CO1)
4. (a) Discuss the importance of Hardwired and micro programmed control unit. (CO1)
- OR
- (b) Explain Instruction Cycle. Draw the flow-chart of Fetch, and Decode instruction. (CO1)
5. (a) Discuss Booth multiplication algorithm. Draw and explain the flowchart to support your answer. (CO2)

OR

- (b) Implement following circuits using Decoder : (CO2)
- (i) Full adder
  - (ii) Full Subtractor

TMC-102

700