

Roll No.

|  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|

H

## TEC-201

### B. Tech. (Second Semester) End Semester EXAMINATION, 2017

(All Branches)

#### BASIC ELECTRONICS ENGINEERING

*Time : Three Hours ]*

*[ Maximum Marks : 100*

**Note :** (i) This question paper contains *five* questions.

(ii) All questions are compulsory.

(iii) Instructions on how to attempt a question are mention against it.

(iv) Total marks assigned to each question are twenty.

1. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) What is Duality principle of Boolean algebra ? State and prove the DeMorgan's laws.

(b) Perform the following number system conversion :

(i)  $(65.2)_8 = (?)_{10}$

[ 2 ]

TEC-201

(ii)  $(A9.8)_{16} = (?)_{10}$

(iii)  $(85.25)_{10} = (?)_2$

(iv)  $(111011.100)_2 = (?)_8$

(v)  $(10100111)_2 = (?)_{16}$

(c) Perform the following :

(i)  $(35)_{10} + (25)_{10}$  in Binary

(ii)  $(389)_{10} + (245)_{10}$  in BCD

(iii)  $(13)_{10} - (10)_{10}$  in Binary using 1's complement

2. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Write short notes on the following :

(i) Extrinsic semiconductors

(ii) Mass action law

(b) Derive the continuity equation for semiconductors

(c) A semiconductor has  $10^{16}/\text{cm}^3$  donor atom concentration and  $1.1 \times 10^{17}/\text{cm}^3$  acceptor atom concentration. If intrinsic carrier concentration is  $10^{12}/\text{cm}^3$ , then find the free electron and hole concentration and conductivity if mobility of electron is  $800 \text{ cm}^2/\text{V-s}$  and that of hole is  $200 \text{ cm}^2/\text{V-s}$ .

A-76

[ 3 ]

TEC-201

3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) What do you mean by the breakdown of a PN junction diode ? Discuss the effect of temperature on the characteristics of PN junction diode.

(b) Derive the expression for ripple factor, rectification efficiency and PIV for a centre tapped full wave rectifier.


(c) Write short notes on the following :

(i) Varactor diode

(ii) LED

4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)(a) Draw CB, CE and CC configuration of a BJT. Discuss the currents  $I_{CBO}$  and  $I_{CEO}$ .

(b) Explain construction, operation and characteristics of an E/MOSFET.

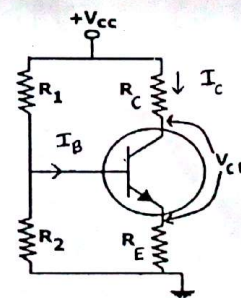(c) In the following circuit find  $I_C$  and  $V_{CE}$ . Given  $V_{CC} = 12 \text{ V}$ ,  $R_1 = 12 \text{ k}\Omega$ ,  $R_2 = 2.4 \text{ k}\Omega$ ,  $R_C = 3.8 \text{ k}\Omega$ ,  $R_E = 1 \text{ k}\Omega$ ,  $V_{BE} = 0.7 \text{ V}$  and  $\beta = 50$ .

A-76

P. T. O.

5. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Write short notes on the following :

- (i) Concept of virtual ground
- (ii) Properties of an ideal Op-amp

(b) Derive expression for voltage gain of :

- (i) Inverting
- (ii) Non-inverting operational amplifier configurations

(c) Determine output voltage  $V_o$  in the following circuits :

