

Roll No.

--	--	--	--	--	--	--

H

TEE-101

**B. Tech. (First Semester)
End Semester EXAMINATION, 2017
(All Branches)**

BASIC ELECTRICAL ENGINEERING

Time : Three Hours] [Maximum Marks : 100

Note : (i) This question paper contains *five* questions.

(ii) All questions are compulsory.

(iii) Instructions on how to attempt a question are mention against it.

(iv) Total marks assigned to each question are **twenty**.

1. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)


(a) Define the statement of Norton's theorem and Thevenin's theorem with its equivalent circuit.

(b) What is analogy between electrical and magnetic circuit ? Draw series and parallel magnetic circuit with mathematical expression for m.m.f., flux and magnetic field intensity.

[2]


TEE-101

- (c) In the below given circuit determine current across resistance R_L for $R_L = 1, 2$ and 3 ohm using Thevenin's theorem.

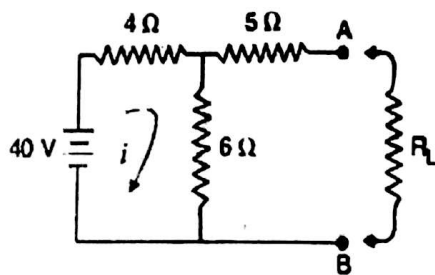

2. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

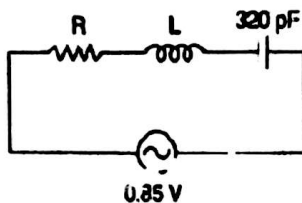- (a) In three-phase can we obtain three-phase power in star or delta circuit by two wattmeter method ? If yes, then derive the expression for active power.
- (b) For the circuit shown determine the value of inductance for resonance if $Q = 50$ and $f_a = 175$ kHz. Also find the circuit current the voltage across the capacitor and the bandwidth of the circuit.



C-47

[3]

TEE-101

- (c) Derive the condition obtained in case of resonance in series RLC circuit and also derive expression for quality factor in series RLC circuit.

3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

- (a) (i) What is the principle of Faraday law of electromagnetic induction for static e.m.f. ?
- (ii) Which electrical device have working e.m.f. in terms of static e.m.f. ?
- (iii) Obtain mathematical expression and draw with complete equivalent circuit of transformer when primary referred to secondary side.
- (b) Determine the efficiency of a 150 kVA transformer at 25%, 33% and 100% full-load (i) At unity p. f. (ii) At 0.8 p. f. lag if the copper loss is 1600 W at full-load and the iron loss is 1400 W.
- (c) Explain O. C. and S. C. test of single-phase transformer with its equivalent circuit.

4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

- (a) Define the following :
- (i) Bilateral and Non-linear element


C-47

P. T. O.

[4]

TEE-101

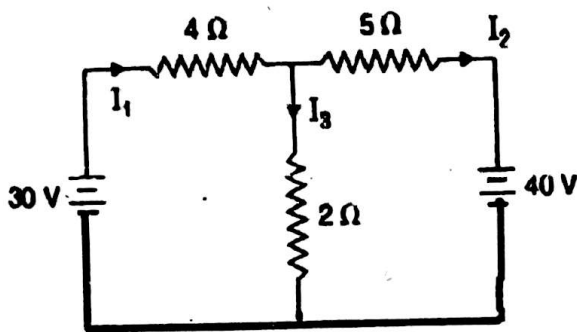- (ii) Bandwidth
- (iii) Form Factor and average value
- (iv) Time period and frequency
- (b) Using NODAL analysis determines all branch currents.



- (c) Define maximum power transfer theorem for d.c. circuit and derive the condition of maximum efficiency.
- 5. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
 - (a) (i) What is the principle of D.C. machine with its construction diagram ?
 - (ii) Derive expression for resultant m.m.f. in three-phase rotating magnetic field.
 - (b) The power into a balanced 3-phase inductive load measured by two wattmeters are

C-47

[5]

TEE-101

- 1500 W and 1000 W. The line voltages are 440 V, 50 Hz. Determine the active power, reactive power, kVA and power factor of the load.
- (c) The power input to the rotor of a 440 V, 50 Hz, 6-pole, 3-phase induction motor is 100 kW. The rotor electromotive force is observed to make at 960 r. p. m.
Calculate :
 - (i) The slip.
 - (ii) The rotor speed
 - (iii) Speed of stator field with respect to rotor.
 - (iv) Frequency of rotor current at standstill.
 - (v) Speed of rotor magnetic field with respect to stator magnetic field.

TEE-101

590

C-47