

B.Tech Mid Semester Examination 2023
I Semester
Basic Electronics Engineering (TEC-101)

Time: 1:30 Hours

MM: 50

NOTE: Answer all questions by choosing any one of the sub questions (either part a or part b)

Each question carries 10 marks

Q.1 (a)

CO 1

Perform the following number system conversions:

(i) $(+5)_{10} = (?)_{16}$

(ii) $(11001010)_2 = (?)_{10}$

(iii) $(789)_{10} = (?)_{16}$

(iv) $(33)_{10} - (13)_{10}$ in Binary using 1's complement.

(v) $(12)_{10} - (20)_{10}$ in Binary using 2's complement.

OR

Q.1 (b)

CO 1

What are universal logic gates and why they are called so? Realize the following:

(i) X-OR gate using NAND gates.

(ii) $AB + A'B'C + AB'C$ using NAND gates.

Q.2 (a)

CO 1

(i) State and prove DeMorgan's laws of Boolean Algebra.

(ii) Realize the following Boolean functions using basic gates:

(i) $A + B.C$

(ii) $\overline{B}.C + \overline{A}.B$

(iii) $(A+B).C$

OR

Q.2 (b)

CO 1

Write short notes on the topics given below:

(i) SOP and POS form of logic expression

(ii) canonical form of logical expression

Q.3 (a)

CO 1

Solve the following expression using K-Map and realize the logic circuit using basic gates.

$$F(A,B,C,D) = \sum m(0, 2, 4, 6, 9, 12) + \sum d(1, 14)$$

OR

Q.3 (b) For the given truth table, express output Y in minimized SOP and minimized POS form. CO 1

| X | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Q.4

(a)

CO2

What is significance of doping in semiconductors. With the help of neat diagram explain formation of n type semiconductor by doping.

Calculate the drift current produced in an intrinsic Ge semiconductor having area of cross section 2 cm^2 and length 10 cm . If concentration of free electron is $2 \times 10^{19}\text{ m}^{-3}$ and a battery of 2 Volts is applied across its length. Given that mobility of free electrons and holes is $0.36\text{ m}^2/\text{V-sec}$ and $0.17\text{ m}^2/\text{V-sec}$ respectively.

OR

Q.4 (b) Briefly explain mass action law in semiconductors.

CO2

Assuming that the two diodes D1 and D2 used in the electric circuit shown in the figure are ideal. Find out the value of the current flowing through 1Ω resistor.



Q.5 (a)

CO2

Define following:

- Mobility
- Conductivity
- Drift velocity
- Drift and Diffusion currents

OR

Q.5 (b)

CO2

Explain how a depletion region is formed in a junction diode. How does its width change when the junction is:

- forward biased, and
- reverse biased

A Si diode has reverse saturation current of $2.5\mu\text{A}$ at room temperature. Determine forward voltage to obtain a forward current of 10 mA .