

B.Tech End Semester Examination-2024

Name of the course: B.Tech

Name of the Paper: Basic Electrical Engineering

Time: 3:00 Hrs

Semester: II

Course Code: TEE-201

Maximum Marks: 100

Note:


- (i) All questions are compulsory.
- (ii) Answer any two sub questions among a, b and c in each main question.
- (iii) Total marks in each main question are twenty.
- (iv) Each question carries 10 marks.

Q1

(10 * 2 = 20 marks)


a)

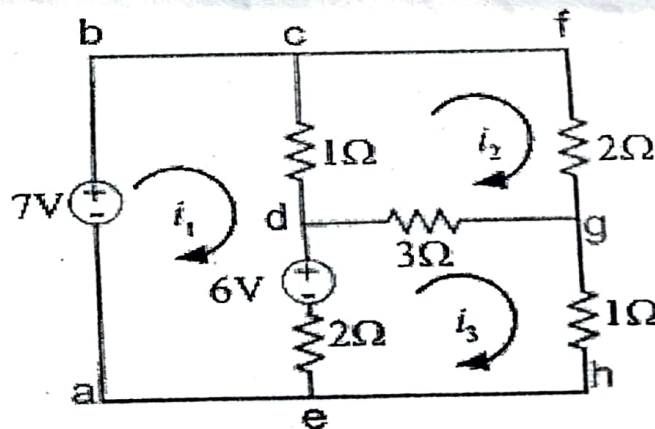Using mesh analysis, Find the value of the currents i_1 , i_2 and i_3 flowing clockwise in the first, second and third mesh respectively.




b)

Calculate Current in 6 ohm using nodal analysis.

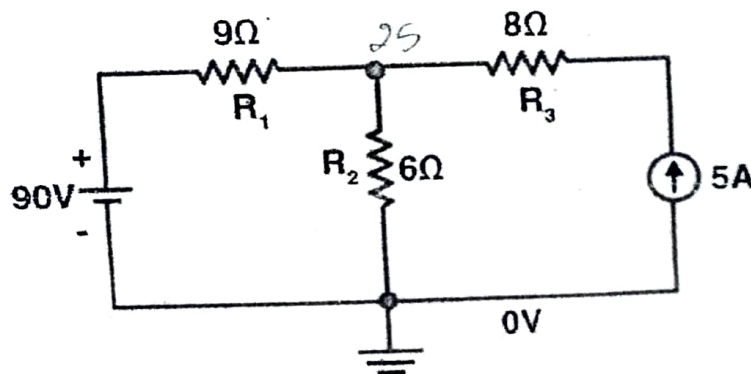

CO1

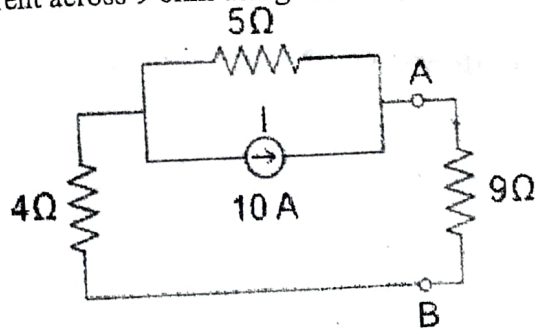
- c) Calculate current across 9 ohm using Norton's theorem.



(10 * 2 = 20 marks)

Q2

- a) Calculate the current through the load resistance (R_4) = 3 Ω using Thevenin's theorem.

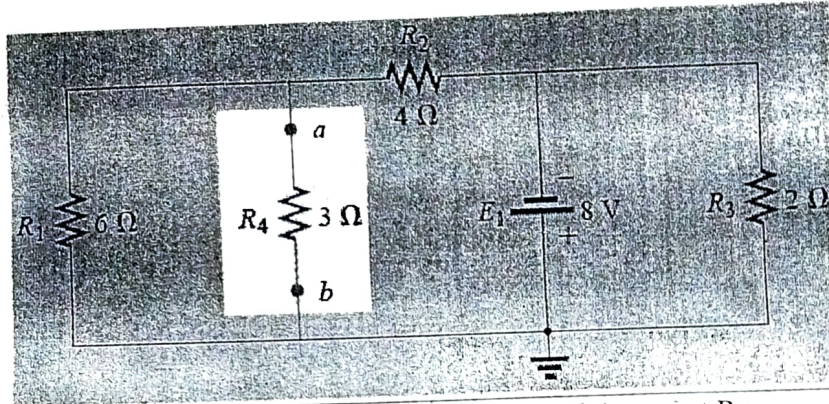

CO2

- b) i) What is power? Define Active, Reactive and Apparent Power with Power triangle.
ii) A motor draws 5 A when supplied from a 110 V AC supply. The power factor is 0.8 lagging. What is the power consumed by the motor?

- c) Explain power factor with its significance in AC.

(10 * 2 = 20 marks)

Q3

- a) A capacitor and 50-ohm resistances are connected in series to an alternating current supply. The voltage across the capacitor is 200 V RMS and across the resistor is 150 V RMS. Determine:

- i) RMS value of supply voltage
ii) Peak value of the voltage across capacitor assuming sine wave

- b) A circuit consists of a coil of resistance 100 ohm and inductance 1H in series with capacitor of 1 μF. calculate
i) Resonant frequency
ii) Current at resonant frequency
iii) Voltage across each element when the supply voltage is 50v.

CO2

- c) Explain with the help of diagram what you understand by in phase, lagging and leading as applied to sinusoidal quantities.

(10 * 2 = 20 marks)

Q4

- a) Explain the working of MCB in detail.

CO3

- b) Write short notes on following:
i) Earthing

| | | |
|----|---|------|
| | ii) SFU iii) DPDT switch iv) Conduit wiring | |
| c) | Define Batteries, type and characteristics of batteries, also differentiate between primary and secondary batteries. | |
| Q5 | (10 * 2 = 20 marks) | |
| a) | A 4-pole wave Connected DC generator has 220 coils of 10 turns each. The speed is 400 rpm. If the machine has a useful flux of 0.05 Wb, find the generated EMF. | |
| b) | Design and explain a circuit to control single lamp load from two locations. | CO4, |
| c) | Define following: i) Faraday's law ii) Slip iii) Fleming's left-hand rule iv) Rotating magnetic field | CO5 |