

Roll No.

--	--	--	--	--	--	--

H

**TEE-201**

**B. Tech. (Second Semester)**  
**End Semester EXAMINATION, 2017**

**(All Branches)**

**BASIC ELECTRICAL ENGINEERING**

*Time : Three Hours ] [ Maximum Marks : 100*

**Note :** (i) This question paper contains *five* questions.

(ii) All questions are compulsory.


(iii) Instructions on how to attempt a question are mention against it.

(iv) Total marks assigned to each question are **twenty**.

1. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) State Norton's Theorem and explain this theorem with steps from any example.

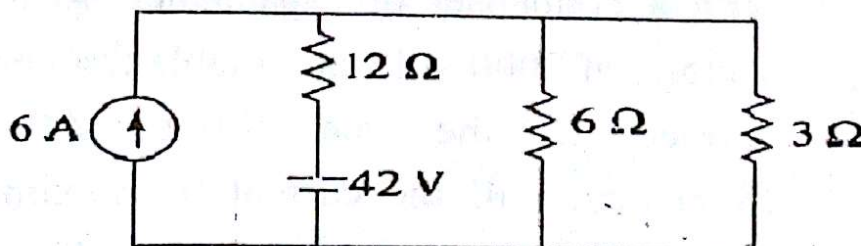
(b) Find the current through the  $3\ \Omega$ .



[ 2 ]

TEE-201

- (c) The value of the resistance  $R$  connected across the terminals A and B, which will absorb the maximum power is :

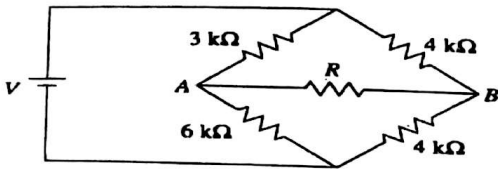

2. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Define the following :

- (i) Linear and non-linear element
- (ii) Quality factor
- (iii) r. m. s. and average value
- (iv) Time period and frequency

- (b) A coil having resistance of 10 ohm and an inductance of 0.4 H is connected in series with a condenser of capacitance 40 mF. A voltage of 2000 volts at variable frequency is applied to the combination. At what frequency, will the current be maximum ? Calculate this current and find quality factor and bandwidth of this circuit.

A-76

[ 3 ]

TEE-201

- (c) Derive the condition of response in series RLC circuit and also derive expression for quality in series RLC circuit.

3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

- (a) (i) What is the principle of single phase transformer ?
- (ii) What is the analogy between electrical and magnetic circuit ?
- (iii) Draw a complete equivalent circuit of transformer with secondary referred to primary side.
- (b) The power into a balanced 3-phase inductive load measured by two wattmeter's are 2000 W and 1000 W. The line voltages are 400 V, 50 Hz. Determine the active power, reactive power, kVA and power factor of the load.
- (c) Explain all type of losses in the transformer during its operation at full load.

4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

- (a) Prove that active and reactive power in three phase balanced star circuit can be measured by two Wattmeter method.

A-76

P. T. O.

[4]

TEE-201

- (b) A 40 kVA transformer has iron loss of 450 W and full-load copper loss of 850 W. If power factor of the load is 0.8 lagging. Calculate :
- full-load efficiency
  - the load at which maximum efficiency occurs
  - the maximum efficiency
- (c) Define Maximum power transfer theorem for d. c. circuit and derive the condition of maximum efficiency.
5. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- What is the principle of DC machine with its construction diagram ?
    - Write the different classification of d. c. motor.
  - The armature of a four-pole, lap-wound shunt generator has 120 slots with 4 conductors per slot. The flux per pole is 0.05 Wb. The armature resistance is  $0.05 \Omega$  and the shunt-field resistance is  $50 \Omega$ . Find the speed of the machine when supplying 450 A at a terminal voltage of 250 V.
  - The power input to the rotor of a 440-V, 50 Hz, 6-pole, 3-phase induction motor is

A-76

[5]

TEE-201

- 100 kW. The rotor electromotive force is observed to make at 1000 r. p. m. Calculate :
- The slip
  - The rotor speed
  - Speed of stator field with respect to rotor
  - Frequency of rotor currents at standstill
  - Speed of rotor magnetic field with respect to stator magnetic field.

TEE-201

580

A-76