

H

Roll No.

TCS-301

B. TECH. (CSE) (THIRD SEMESTER) MID SEMESTER EXAMINATION, 2022

LOGIC DESIGN

Time : 1½ Hours

Maximum Marks : 50

Note : (i) Answer all the questions by choosing any *one* of the sub-questions.

(ii) Each question carries 10 marks.

1. (a) (i) Find the $(r - 1)$'s of $(6652312)_7$. () 2
- (ii) What is binary equivalent of $(0.125)_{10}$? () 2
- (iii) Find the $(111111101)_2 = ()_{10}$ 2
- (iv) $(11011.110)_2 = ()_8$ 2
- (v) Find the r 's complement of $(544663)_7$. () 2 (CO1)

P. T. O.

OR

(b) (i) Represent the decimal number 2545 in (I) BCD, (II) Excess-3 code. 3

(ii) Express the Boolean function $F(A, B, C) = A + BC$ using sum of minterm. 3

(iii) Simplify the Boolean function using k-map : 4 (CO1)

$$f(a, b, c, d, e) = \sum (0, 1, 2, 3, 5, 6, 10) + \sum_d (8, 12)$$

2. (a) (i) The Hamming code 1111110 is received as even parity. Correct error if any. 3

(ii) Given $\sqrt{(222)_r} = (13)_r$, find the value of radix r . 3

(iii) Perform the following arithmetic operation using 1's complement : 4 (CO3)

(I) Add $(11)_{10}$ and $(12)_{10}$

(II) Add $(-39)_{10}$ and $(49)_{10}$

OR

(b) (i) Design a 3-bit combinational circuit which produces logic 1 output when more than input is greater than 011. 5

(ii) With the use of K-map, find the simplest SOP form of the function $F = f.g.$, where $f(a, b, c, d) = abc' + ac'd'$ and $g(a, b, c, d) = (a + b + c' + d)(b' + c' + d)$. 5 (CO1)

3. (a) (i) Given the two numbers $X = 84$ and $Y = 67$, perform the subtraction : 5

(I) $X - Y$

(II) $Y - X$

using 2's complements.

(ii) Simplify the Boolean function and implement using NOR gate only :

5 (CO1)

$$f(a, b, c, d) = \sum (1, 3, 10, 14, 15) + \sum_d (0, 2)$$

P. T. O.

OR

- (b) (i) Write the Boolean equation for function T1 and draw the logic diagram of the circuit containing minimum gates whose outputs are defined by the following truth table : 5

A	B	C	T1
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	1	0	0
1	1	1	1

- (ii) $Y = \Sigma m (3, 5, 7, 8, 10, 11, 13)$
minimize the expression using Quine
Mc-Cluskey method. 5 (CO1)

4. (a) Design four-bit magnitude comparator and draw its logic gate implementation.

10 Marks (CO2)

OR

- (b) Simplify the following functions using Boolean algebra : 10 Marks (CO2)

$$(i) F = B \cdot (A + B)$$

$$(ii) F = \bar{A} + \bar{B} + A \cdot B$$

$$(iii) F = [AB'(C + BD) + A'B']C$$

5. (a) Simplify the following function using SOP and POS forms : 10 Marks (CO3)

$$F(A, B, C, D, E) = \sum m(0, 5, 6, 8, 9, 10, 11, 16, 20, 24, 25, 26, 27)$$

OR

- (b) Implement the following Boolean function using 4×1 multiplexer and external logic gates : 10 Marks (CO3)

$$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$$

$$F(A, B, C, D) = \sum(1, 2, 5, 7, 8, 11, 12, 13, 15)$$