

H

Roll No. 2299038

TCS-308

B. TECH. (CSE) (THIRD SEMESTER)

END SEMESTER

EXAMINATION, Oct., 2023

LOGIC DESIGN AND COMPUTER

ORGANIZATION

Time : 1½ Hours

Maximum Marks : 50

Note : (i) Answer all the questions by choosing any *one* of the sub-questions.

(ii) Each sub-question carries 10 marks.

1. (a) Simplify $F(v, w, x, y, z) = \sum m(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$ using K-map and implement the final output using NAND gates only. (CO1)

P. T. O.

(2)

TCS-308

OR

(b) Simplify the following Boolean function

$$Y(A, B, C, D) = \sum m(0, 5, 7, 8, 9, 10, 11, 14, 15)$$

using Quine-McCluskey minimization technique. Find the prime implicants and essential prime implicants.

(CO1)

2. (a) Realize the $F(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 12, 14)$ using 16 : 1 MUX and also 8 : 1 MUX with a as control variable.

(CO2)

OR

(b) Design a 2-bit magnitude comparator and implement its logic circuit. (CO2)

3. (a) Write any *three* differences between multiplexer and demultiplexer. Construct 16×1 multiplexer with two 8×1 multiplexer and one 2×1 multiplexer.

(CO3)

OR

- (b) With the help of decoder and external logic gates, design the combinational circuit defined by the following three Boolean functions : (CO3)

$$F_1 = (\bar{y} + x)z$$

$$F_2 = \bar{y}\bar{z} + x\bar{y} + y\bar{z}$$

$$F_3 = (\bar{x} + y)z$$

4. (a) A sequential circuit with two D flip-flops, A and B; two input x and y ; and one output z , is specified by the following next-state and output equations : (CO3)

$$A(t' + 1) = x'y + xA$$

$$B(t' + 1) = x'B + xA$$

$$z = B$$

- (i) Draw the logic diagram for the circuit
(ii) Derive the state table.

OR

- (b) Discuss the problems of JK flip-flop. Do the following flip flop conversions : (CO3)

- (i) D flip-flop to SR flip-flop
(ii) T flip-flop to J-K flip-flop

(4)

TCS-308

5. (a) Explain the design procedure for synchronous sequential circuits design with suitable example. (CO2)

OR

- (b) Reduce the number of states in the following state table and tabulate the reduced state table and state diagram :

(CO2)

Present State	Next State		Output	
	$x = 0$	$y = 0$	$x = 0$	$y = 0$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1