

12/12/16

Roll No.

--	--	--	--	--	--	--

H

TEE-101

B. Tech. (First Semester)
End Semester EXAMINATION, 2016

(All Branches)

BASIC ELECTRICAL ENGINEERING

Time : Three Hours]

[Maximum Marks : 100

Note : (i) This question paper contains five questions.

(ii) All questions are compulsory.


(iii) Instructions on how to attempt a question are mentioned against it.

(iv) Total marks assigned to each question are twenty.

1. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) State KCL, KVL and Ohm's law in detail.

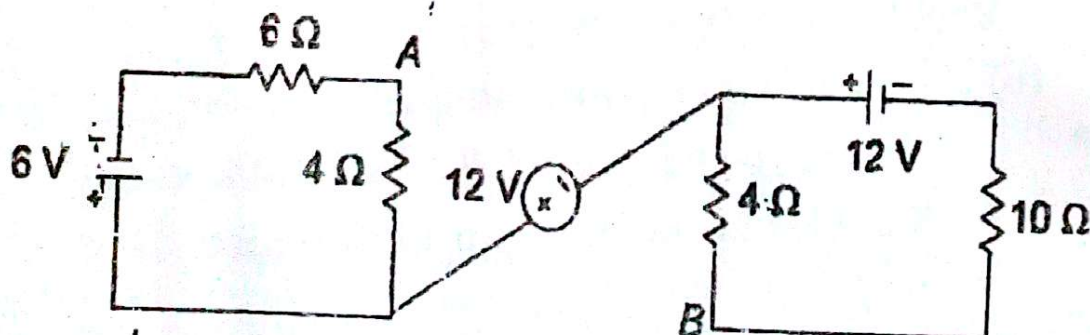(b) What is the voltage across A and B in the circuit shown in Fig.



D-50

P. T. O.

[2]

TEE-101

- (c) State Thevenin's theorem. Explain with a suitable example.
2. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Define the following terms with example :
- Peak factor
 - Form factor
 - Quality factor
- (b) A series RLC circuit with $R = 10$ ohms, $L = 10$ mH and $C = 1$ mF has an applied voltage of 200 V at resonant frequency. Calculate the resonant frequency, the current in the circuit and the voltages across the elements at resonance. Find also the quality factor and bandwidth.
- (c) Draw Parallel Magnetic Circuit. What is Analogy between Electrical and Magnetic Circuit ?
3. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Explain Hysteresis and Eddy Current loss in alternating field.
- (b) The reading on two wattmeter's connected to measure power are 6.0 kW and 1.0 kW; the latter reading being obtained after reversal of

[3]

TEE-101

- the current in the current coil. Calculate the total power and the power factor of the load.
- (c) What is meant by O. C. and S. C. test in single-phase transformer ? Explain with the help of equivalent circuit.
4. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)
- (a) Explain the principle and construction of D. C. Motor with suitable diagram.
- (b) A 5 kVA 250/500 V, 50 Hz, single-phase transformer gives the following test results :
- | | | | |
|------------------------------|-------|--------|--------|
| No-load test (LV side) | 250 V | 0.75 A | 60 W |
| Short circuit test (HV side) | 9 V | 6 A | 21.6 W |
- Calculate :
- Find the value of x (load factor) for which maximum efficiency obtained.
 - Determine efficiency for half load at 0.8 p.f. lagging.
- (c) Prove that total power in three phase balanced circuit can be measured by two wattmeter method.

5. Attempt any *two* questions of choice from (a), (b) and (c). (2×10=20 Marks)

(a) Explain the concept of three-phase Rotating Magnetic Field

(b) A d. c. shunt machine connected to 250 V supply has resistance of armature as 0.1 and of field winding as 100. Find the ratio of the speed as a generator to the speed as a motor when the line current in each case is 80 A.

(c) A parameter load is to be driven at about 700 r. p. m. What should be the number of poles for a 3- ϕ induction motor when :

(i) $f = 60$ Hz ?

(ii) $f = 50$ Hz ?

Calculate the actual speed in each case if the rated slip is 4%.